

ECE 385 Experiment 5 CPU

Viraj Shitole, Ethan Chow

4 March, 2023

0.1 Introduction

In this experiment we design a simple microprocessor cpu implementing the 16 bit LC-3 ISA. The LC-3 is a reduced instruction set ISA designed for use in computer architecture education. Although largely superseded by modern RISC ISA such as RISC-V or MIPS which have equally easy learning curve, but have more applicable to the real world, it can still teach us the basics of simple CPU design such as datapath, control FSM, register file, fetch decode execute stage, and more.

0.2 Written description

0.2.1 Summary of operation

In our simple single cycle processor, each cycle can be conceptually broken down into three stages, fetch, decode, execute. The fetch stage is made up of states 18, 33(including waiting states), 35. During the fetch phase the contents of the instruction pointer are loaded into instruction register IR. The decode stage is represented by state 32 and it uses the opcode to decide which the next state will be. Finally the rest of the states represent the execute stage. In this stage the opcode is evaluated and any memory operations are written into memory. After the completion of this phase the control unit returns to state S_18 the beginning of the fetch phase.

0.2.2 Top level block diagram

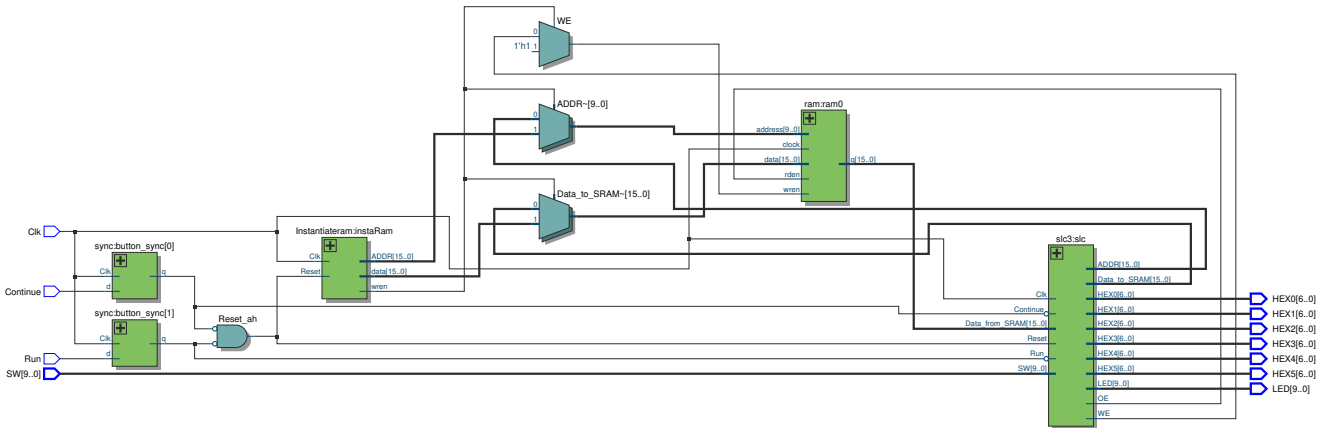


Figure 1: top level block diagram including MMIO and dedicated SRAM

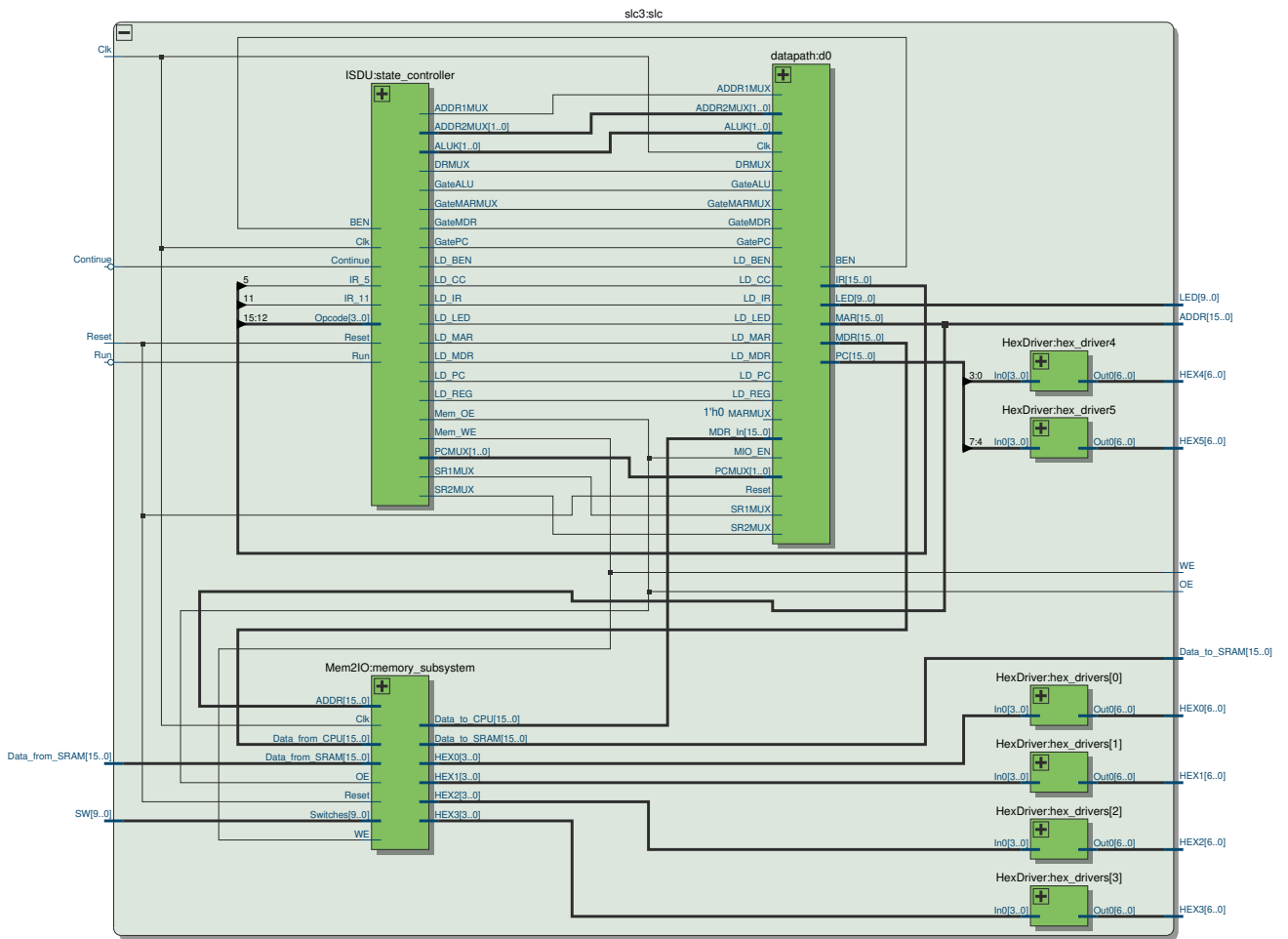


Figure 2: cpu block diagram not including memory and IO

0.2.3 State Diagram for Control Unit

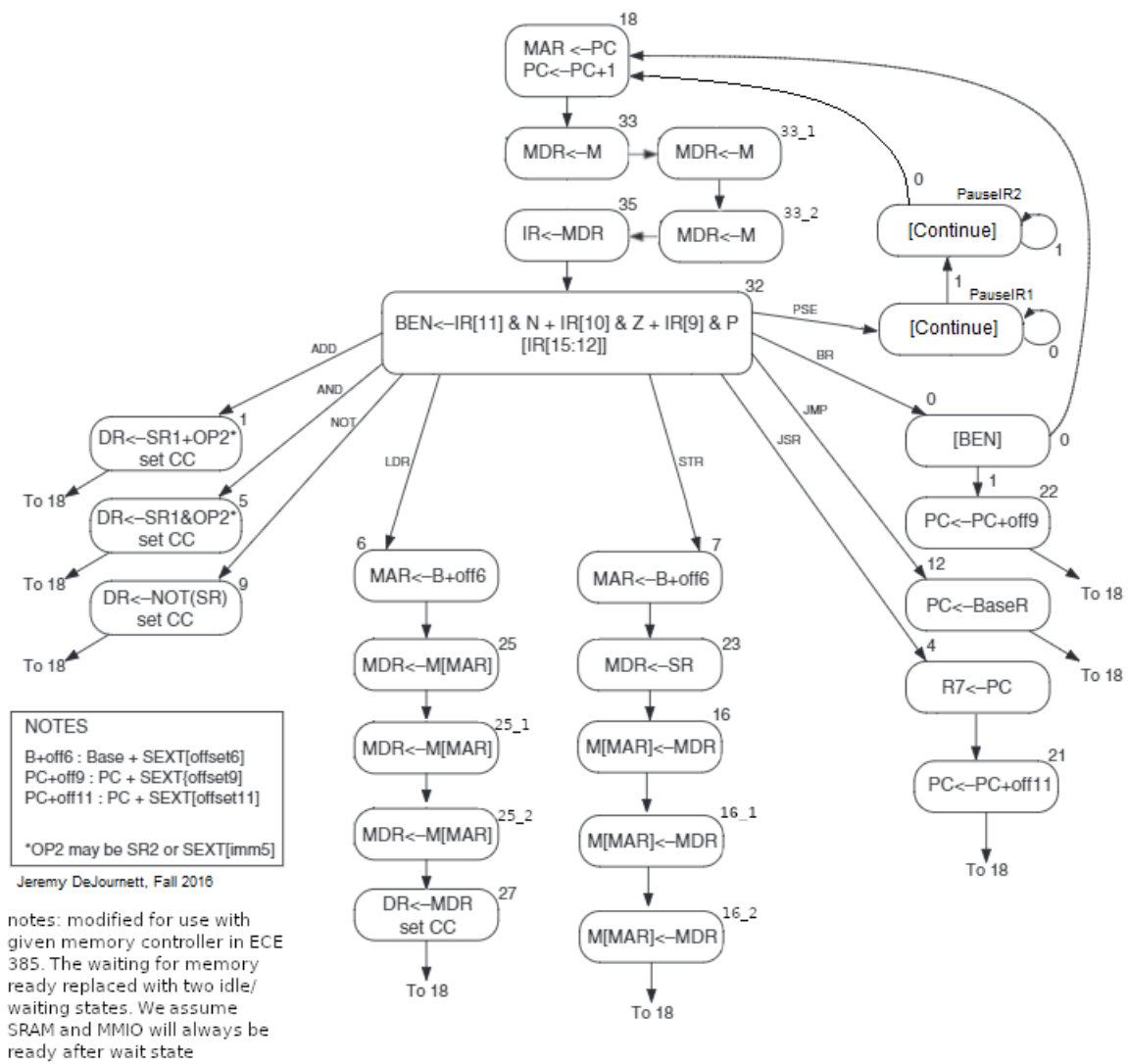


Figure 3: simplified control unit state diagram. the outputs of each state are not shown and are instead listed below.

0.2.4 CPU control FSM description

We implement a single cycle control unit using finite state machine. The outputs of the control unit depend on the current state and are listed below:

```
S_18 : //base register B IR[8:6]
      GatePC = 1'b1;
      LD_MAR = 1'b1;
      PCMUX = 2'b00;
      LD_PC = 1'b1;
S_33_1 : //MDR <= M
      Mem_OE = 1'b1;
S_33_2 : //MDR <= M
      Mem_OE = 1'b1;
S_33_3 :
      Mem_OE = 1'b1;
      LD_MDR = 1'b1;
S_35 :
      GateMDR = 1'b1;
      LD_IR = 1'b1;
PauseIR1: // LEDs <= ledVect12
      LD_LED = 1'b1;
PauseIR2: ; // Wait on Continue
S_32 :
      LD_BEN = 1'b1;
S_01 : //ADD
      SR2MUX = IR_5; // sel imm5
      ALUK = 2'b00; // add
      GateALU = 1'b1;
      LD_REG = 1'b1;
      LD_CC = 1'b1;
      SR1MUX = 1'b0; //IR[8:6]
      DRMUX = 1'b1;
S_00: LD_BEN = 1'b1;
S_04:
      GatePC = 1'b1;
      LD_REG = 1'b1;
      DRMUX = 1'b0; // 111 R7
S_05: //AND
      SR2MUX = IR_5;
      ALUK = 2'b01; //AND
      GateALU = 1'b1;
      LD_REG = 1'b1;
      LD_CC = 1'b1;
      SR1MUX = 1'b0; //IR[8:6]
      DRMUX = 1'b1; //IR[11:9]
S_06, S_07: //MAR <= B + off6
      LD_MAR = 1'b1;
      SR1MUX = 1'b0; // IR[8:6]
      ADDR1MUX = 1'b1; //SR1_OUT
      ADDR2MUX = 2'b01; //offset6
      GateMARMUX = 1'b1;
S_09: //NOT R(DR) <= ~R(SR1)
      SR2MUX = IR_5;
      ALUK = 2'b10; //alu_out = ~A
      GateALU = 1'b1;
      LD_REG = 1'b1;
      LD_CC = 1'b1;
      SR1MUX = 1'b0; //IR[8:6]
      DRMUX = 1'b1; //IR[11:9]
S_12: //JMP PC <= BaseR
      SR1MUX = 1'b0; //IR[8:6]
      LD_PC = 1'b1;
      PCMUX = 2'b01; //PC_alu_out
      ADDR2MUX = 2'b01; //IR[5:0]
      ADDR1MUX = 1'b1; //reg_SR1
S_16_1, S_16_2, S_16_3: // M[MAR] <= MDR
      Mem_WE = 1'b1;
S_21: //PC<=PC+off11
      ADDR2MUX = 2'b11; // IR[10:0]
      off11
      PCMUX = 2'b01; // pc_branch
      LD_PC = 1'b1;
S_22: // PC <= PC + off9
      ADDR2MUX = 2'b10; // IR[8:0] off9
      PCMUX = 2'b01; // pc_branch
      LD_PC = 1'b1;
S_23: // MDR <= SR
      ALUK = 2'b11; // A
      SR1MUX = 1'b1; //IR[11:9]
      GateALU = 1'b1;
      LD_MDR = 1'b1;
S_25_1: Mem_OE = 1'b1; // MDR <= M[MAR]
S_25_2: Mem_OE = 1'b1; // MDR <= M[MAR]
S_25_3: // MDR <= M[MAR]
      Mem_OE = 1'b1;
      LD_MDR = 1'b1;
S_27: // DR <= MDR
      LD_CC = 1'b1;
      DRMUX = 1'b1; //IR[11:9]
      GateMDR = 1'b1;
      LD_REG = 1'b1;
```

0.2.5 SystemVerilog Modules

- module `slc3_testtop`

this is the top level module for use with testbench simulation. It uses a simulated SRAM module.
- module `slc3_sramtop`

this is the top level module for use with onboard SRAM on DE10-Lite devboard. It connects the `slc3` module to physical SRAM onboard the devboard since it would not be practical to write simulated behavioural SRAM in verilog.
- module `slc3`

implementation of SLC3 ISA, connects the signals from control unit and datapath together to form the basis of the cpu.
- package `SLC3_2`

this systemverilog package contains parameters to convert assembly opcode to machine language opcode. it effectively is a very simple assembler allowing us to directly write assembly like code in our test memory contents.
- module `register`

N bit paramaterized register. supports parallel input, output. loading on rising edge clock. used for registers other than main register file.
- module `regfile`

8x16 general purpose register file. 3 bits input for DR, SR1, SR2. Used for cpu register file R7:R0
- module `ALU`

Arithmetic logic unit capable of ADD, bitwise AND, bitwise NOT boolean operations.
- module `mux2_1`

paramaterised N bit 2:1 multiplexer used for processor datapath
- module `mux4_1`

paramaterised N bit 4:1 multiplexer used for processor datapath
- module `mux4_1_onehot`

paramaterised N bit 4:1 multiplexer with one hot selection logic. used for data bus.
- module `Instantiateram`

instantiates on chip SRAM memory for use with Mem2IO MMIO controller. SRAM contents initially contain the test programs to verify the correct functionality of the cpu by testing all the opcode instruction.
- module `Mem2IO`

simple memory controller for cpu, implements MMIO(memory mapped IO) at address 0xffff. Reading or writing to memory address 0x0000 to 0xfffe will read or write to physical onboard SRAM. Writing to MMIO address 0xffff results in the value of the source register specified in the store instruction being written to 7 segment display. Reading from MMIO address 0xffff will read the fpga devboard toggle switch SW[9:0] into the destination register specified in load instruction.

The MMIO takes approximately the same amount of time as SRAM access. In a real CPU the MMIO operation may take much longer than DRAM or SRAM fetch or store, and the control unit of cpu must wait for memory ready signal to continue. Our SLC3 memory controller makes tradeoff of simplicity and fewer logic required at the expense of idle time/speed penalty.

- module **datapath**

implements LC-3 ISA datapath

- module **ISDU**

implements control finite state machine for LC-3 CPU. see CPU control FSM for the operating principle and description of FSM.

- module **HexDriver**

The hex driver does an encoding by taking in a 4-bit input and outputting a 7-bit active low output corresponding to one hot encoding of the segments on the 7-segment display.

- module **testbench**

testbench is used to generate RTL simulation waveform. It contains sequential instructions to give inputs to top level module in order to jump to individual test programs. see simulation waveform for the exact programs and instructions tested.

0.3 simulation waveform

 


Figure 4: simulation waveform showing execution of basic IO test program. the 7segment display displays the hexadecimal value of the toggle switch input. You can see the 7segment one hot active low output for each of the digits represent the switch input as well as the switch value loaded into R1 through MMIO.

 


Figure 5: simulation waveform showing execution of basic IO test program with pause state. the 7segment display is updated with hexadecimal value of toggle switch input every time continue is pulled low during pauseIR state. You can see the 7segment one hot active low output for each of the digits represent the switch input as well as the switch value loaded into R1 through MMIO.

0.4 Post Lab

MEM2IO is the memory controller that implements MMIO and SRAM read write functionality. See Mem2IO module description for details regarding its operation, implementation, and design tradeoff between speed and simplicity.

Both the branch (BR), jump (JMP), and jump subroutine (JSR) functions will modify the instruction pointer register (PC), but they are used for different purpose.

The JMP instruction unconditionally jumps to address specified in source register. It is used when unconditionally jump to a address that cannot be expressed as $PC + \text{imm9}$. This can be needed when executing a program from an operating system or shell.

The JSR instruction unconditionally jumps to $PC + \text{imm11}$ and stores the current instruction pointer into R7. This is used when calling subroutine where you must preserve the base instruction pointer in R7 to return after completion of subroutine.

Finally the BR instruction conditionally branches to $PC + \text{imm9}$ based on the condition codes specified in IR[11:9]. This is used for evaluating if statements, loops and similar constructs in high level programming language.

The R signal in the Patt and Patel book LC3 specification is the memory ready signal from the memory controller. As discussed in Mem2IO module description our memory controller does not implement ready signal to reduce complexity. We compensate for the lack of memory ready signal in our control FSM by introducing multiple wait/idle state in every memory operation. We discovered that we need up to four states to account for stable operation in all power/signal integrity condition. This workaround is stable but wastes time where the cpu is idle for longer than necessary when waiting on memory to become ready. A more robust approach would be for the memory controller to output a ready signal when the memory or MMIO data is ready, and the fsm to immediately proceed to the next state when such signal is asserted. This will maintain perfect synchronisation between processor and memory which will be more fast and stable. In addition, if slower MMIO devices are later added, it will be necessary to assert ready signal since the access latency for MMIO and SRAM may be orders of magnitude apart.

0.4.1 performance statistics

LUT	1366
DSP	0
BRAM Memory (bits)	27648
Flip-Flop	823
Frequency(MHz)	108.48
Static Power(mW)	89.95
Dynamic Power(mW)	1.33
Total Power(mW))	100.20

0.4.2 instructions per second calculations

In order to benchmark the performance of our processor design in millions of instructions per second or MIPS(not to be confused with the MIPS ISA) we use the SignalTap integrated logic analyser to capture waveform of the instruction pointer (PC) register during known programs. We can then count the number of instructions executed over a known time frame and use the average of multiple runs and multiple different programs to approximate the MIPS achieved by our design. We cannot use simulator for calculating real world performance because simulation is not able to accurately predict real world performance like a logic

analyser and real hardware(FPGA) can. We discuss ways we can improve the performance of our design in the conclusion.

xor program MIPS

The XOR test program computation instructions (not including the MMIO input instructions) is stored in test memory addresses 0x001a to 0x0029. We can simply subtract the two instruction pointers to see that there are 15 computation instructions because there is no branch or jump instruction in this computation. The computation takes 650 ns to run therefore the xor computation runs at 23.07 MIPS.

 


Figure 10: SignalTap waveform of xor computation running on actual hardware FPGA

multiplication program MIPS

The multiplication test program computation instructions is stored in test memory addresses 0x003a to 0x0047. Including the add-shift loop branch condition there are 104 instructions. The add shift loop runs 8 times regardless of inputs so the number of instructions is constant regardless of input to the program. The computation takes 5.9 μ s to run therefore the multiplication computation runs at 17.63 MIPS.

 


Figure 11: SignalTap waveform of multiplication computation running on actual hardware FPGA

sorting program MIPS

The sorting test program computation instructions is stored in test memory addresses 0x0077 to 0x0089. There are two nested loops both with index $i = 16$. We can conclude that the computation of sorting program takes $0x10 \times 0x10 \times (0x89 - 0x77) = 0x1200 = 4608_{10}$. The computation takes 126 μ s to run therefore the sorting computation runs at 36.57MIPS.



Figure 12: SignalTap waveform of sorting computation running on actual hardware FPGA

From the 3 samples collected we can approximate the average performance of our design to be 25.76 MIPS.

0.5 Conclusion

We were able to achieve a fully functional LC3 microprocessor with all instructions behaving as expected. If we had more time, we would have done some further optimisations to our design to increase performance and stability. For example, we can modify our memory controller to assert a ready signal when the memory or MMIO operation is complete. This will reduce the number of FSM states significantly since we avoid many arbitrary idle waiting states associated with each memory operation, i turn decreasing gate count because we need fewer states to enumerate in the FSM as well simplified next state logic. Another more complicated optimisation of our design can be to use pipelining to speed up the processor with parallel computing.

The lab documentation was reasonably easy to understand for anyone with some background in computer architecture. Some of the multiplexer input might have been slightly unclear which input correspond to which selection, but as long as it is consistent between datapath and control unit the order does not really matter. The memory controller operation was also slightly unclear because we were instructed to use a workaround for lack of memory ready signal, and it was not clear exactly how long the control FSM should wait for memory controller IO to become ready.